


Time Stamping for Diamond

Peter Fischer, Michael Ritzert


Lehrstuhl für Schaltungstechnik und Simulation
Institut für Technische Informatik
Universität Mannheim

Talk Outline

 
- Overview of common circuit concepts for time stamping
- Design issues
- Recent results with a ring oscillator test chip
- Summary and next steps




Overview of Circuit Concepts

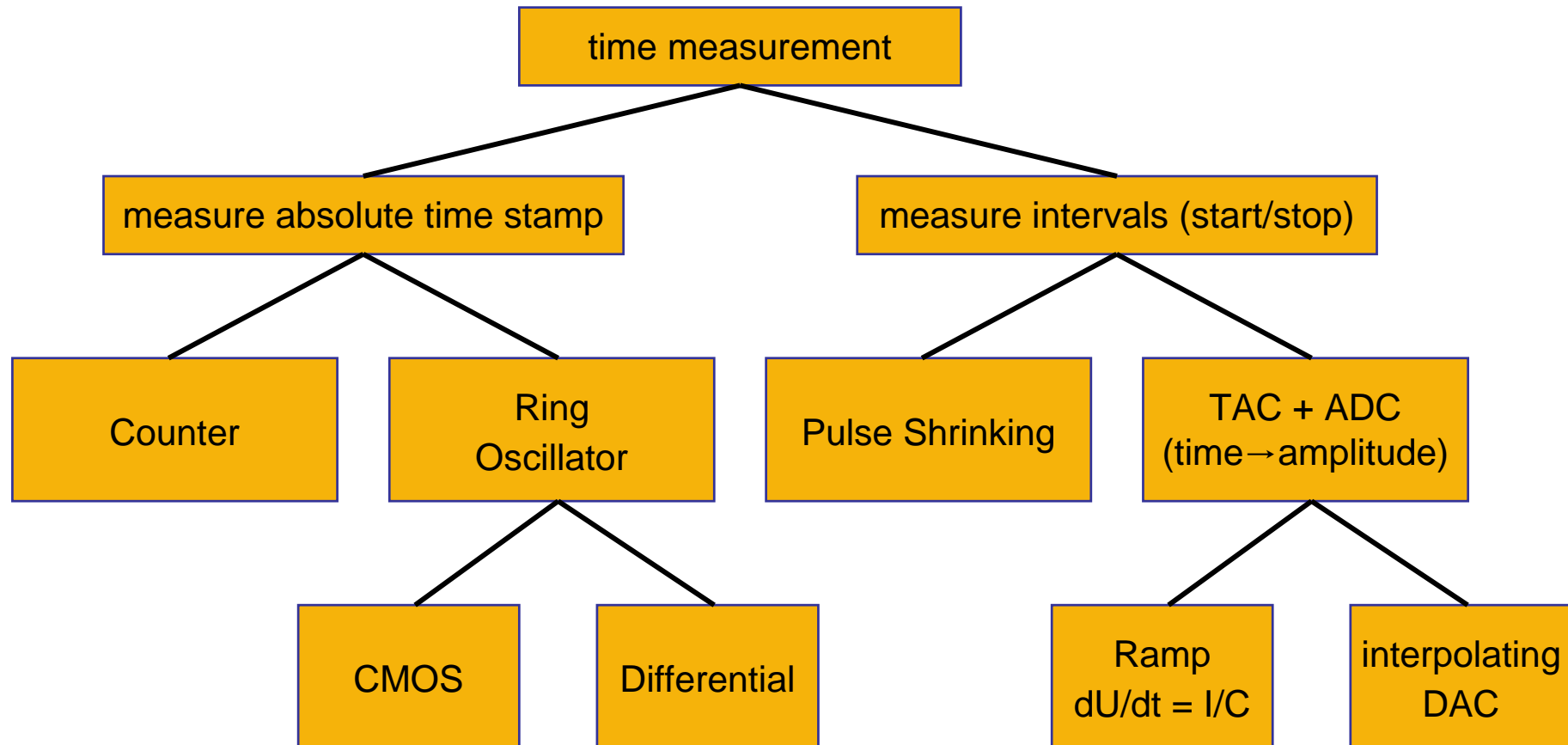


...and mixtures of these concepts

 


Fast Counter

 

 
- Counter must use Gray coding or similar to avoid scrambled bits when latches jitter
- + very simple concept
- + stable and predictable bins
- + low power
- may reach some GHz in 0.18 μ m, i.e. bin widths of some ~200ps
- Improvement with staggering of several counters possible



Ring Oscillator: Principle

 


- Principle:
 - a ring oscillator generates thermometer code time stamps. Needs overall inversion!
 - a ('slow') coarse counter generates the MSBs
 - input signal is used to latch values
 - Ring oscillator can be locked to a reference clock with a PLL
- + fairly simple, 'digital' design
- + infinite dynamic range
- + no calibration required (with PLL), guaranteed stability
- limited bin size (but several times better than with counter)

 


Ring Oscillator: Design variations


- Resolution can be increased by:
 - using multiple channels with delayed stop signals
 - running several phase coupled ring oscillators
 - using slow / fast buffers between ring oscillator and latches
- Use 'single ended' CMOS logic (see Harald Deppe, GSI)
 - simple
 - issues: supply sensitivity, ring oscillator frequency range, linearity (inversion!)
- Use differential logic
 - uncommon
 - more complex, if everything is done differentially
 - trimming simpler

 


Pulse Shrinking

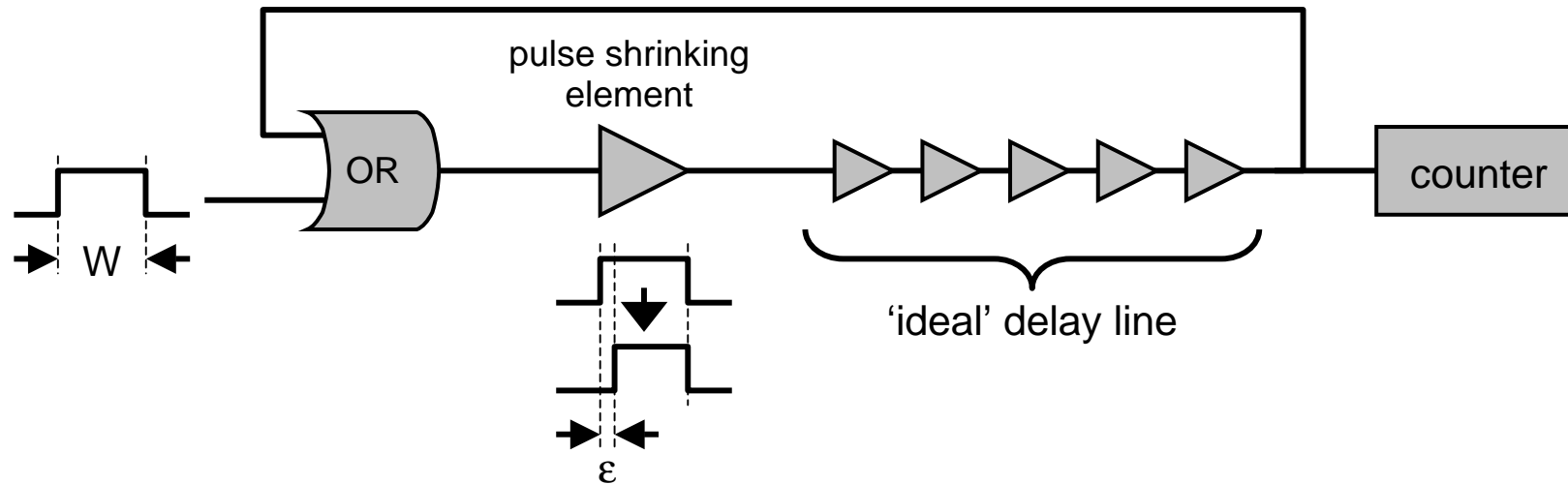



- Principle:
 - Pulse is circulated in an (ideal) delay line.
 - One pulse shrinking element makes pulse shorter by constant ϵ with every 'turn'
 - Width is determined by counting 'turns' until pulse vanishes. $W = N \times \epsilon$
- Delay line must be longer than max. pulse width W_{\max}
- + Very low power
- Conversion time is long and linked to resolution: $T = W_{\max} \times W_{\max} / \epsilon$
- Difficult calibration
- Sensitive to matching and noise (?)

 

TAC + ADC



 


  - Principle:
 - generate a linear voltage ramp during the strobe signal
 - convert the voltage to a digital value with an ADC
 - Ramp can be generated with
 - constant current charging of a capacitor
 - an ‘interpolating DAC’ (see H. Flemming, GSI)
- + very high resolution
- needs ADC
 - extra circuitry needed to generate MSBs
 - Issues are calibration and stability




Differential Logic

- Current I_{bias} is steered to left or right load circuit with a differential pair
- The load circuit converts to current step to a voltage step
- **'ideal' load** circuit:
 - The V_{hi} -level is fixed by the maximum possible input voltage to the switch block ($\sim V_{\text{DD}} - V_{\text{TP}} - V_{\text{DSat}}$)
 - The V_{lo} -level is fixed by the voltage swing required to 'fully' switch current in the switch block. For MOS operated in weak inversion, this is below 200mV!
 - The plateau at $\frac{1}{2} I_{\text{bias}}$ guarantees equal rise and fall times (C_{load} is charged/discharged with $\pm \frac{1}{2} I_{\text{bias}}$)
- If V_{hi} and V_{lo} are independent of I_{bias} , the speed of the gate can be varied significantly with I_{bias}

  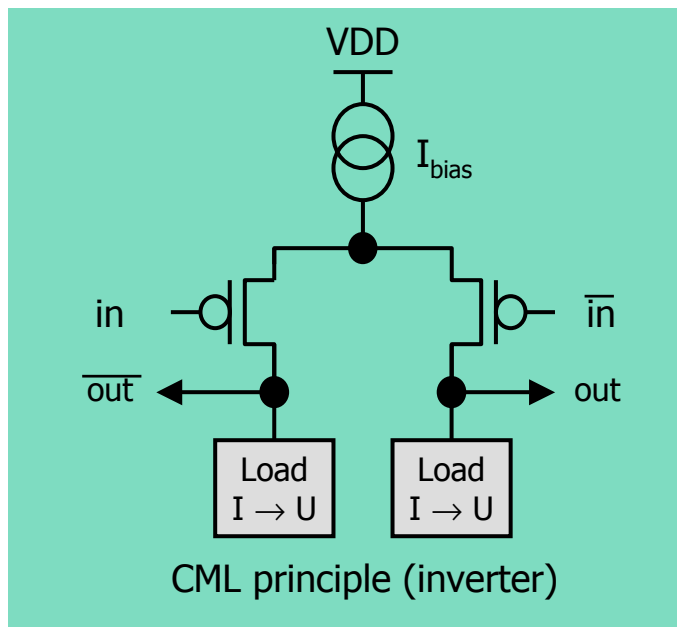



Design Issues

- Design goals are
 - minimal bin width = max. resolution (aim at $\sigma = 50\text{ps}$)
 - linearity
 - dynamic range
 - low dead time = high double hit rate (aim at 10 MHz)
 - low power (not so critical in Diamond: few channels, cooling possible, preamps and discriminators will be 'high' power components)
 - easy calibration
 - stable operation (with temperature, power supply etc.)
 - multi-chip operation (maybe not required for diamond)
- Watch
 - matching between devices:
better for larger devices, but that costs power and/or speed
 - radiation hardness
 - technology scaling (this favors 'digital' designs)

 



AMS 0.35 μ m Test Chip 'TC3'

 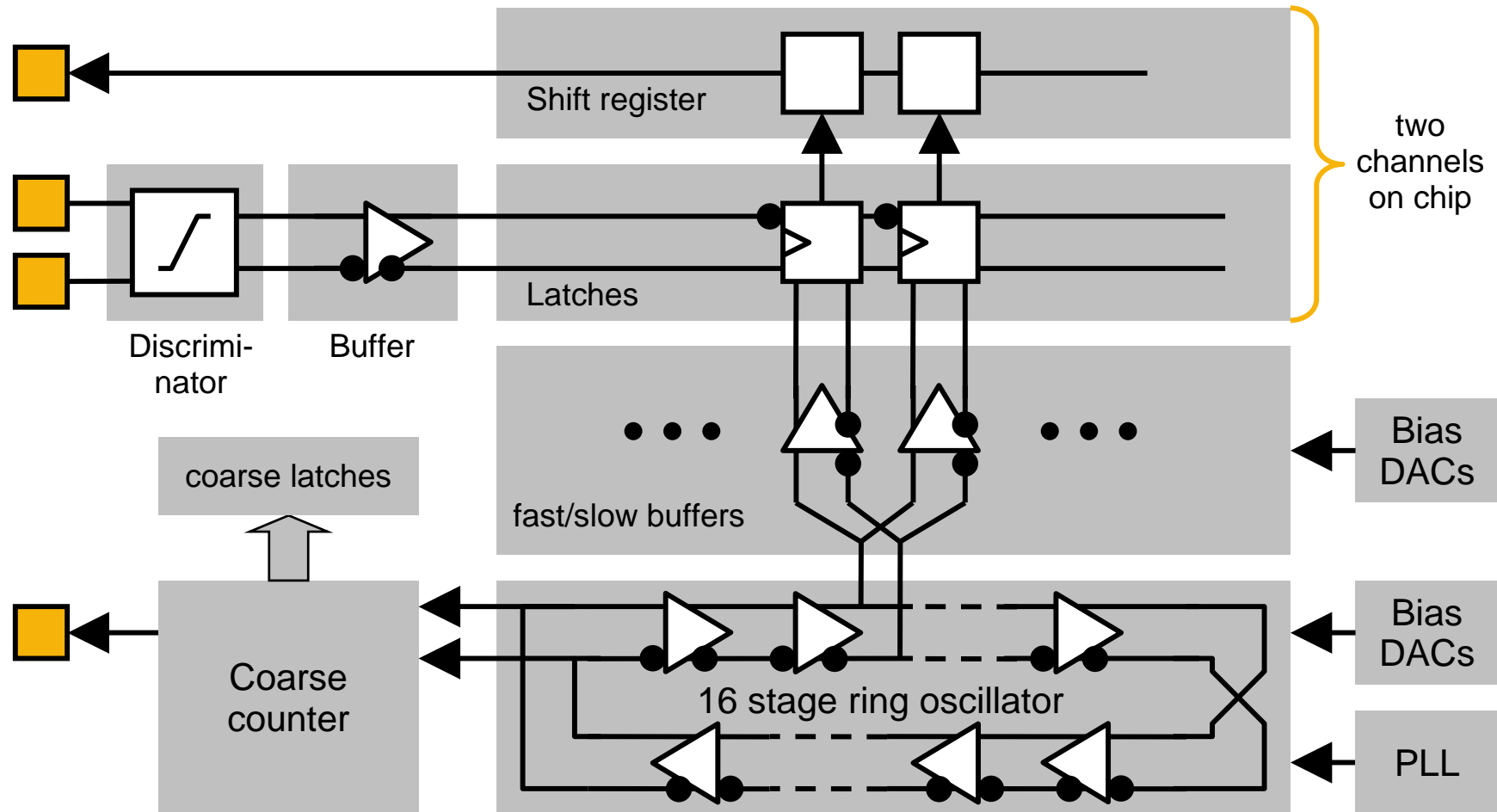- Block diagram shows only relevant parts
- Note that the differential inputs have an additional (analog) discriminator





Test Setup

 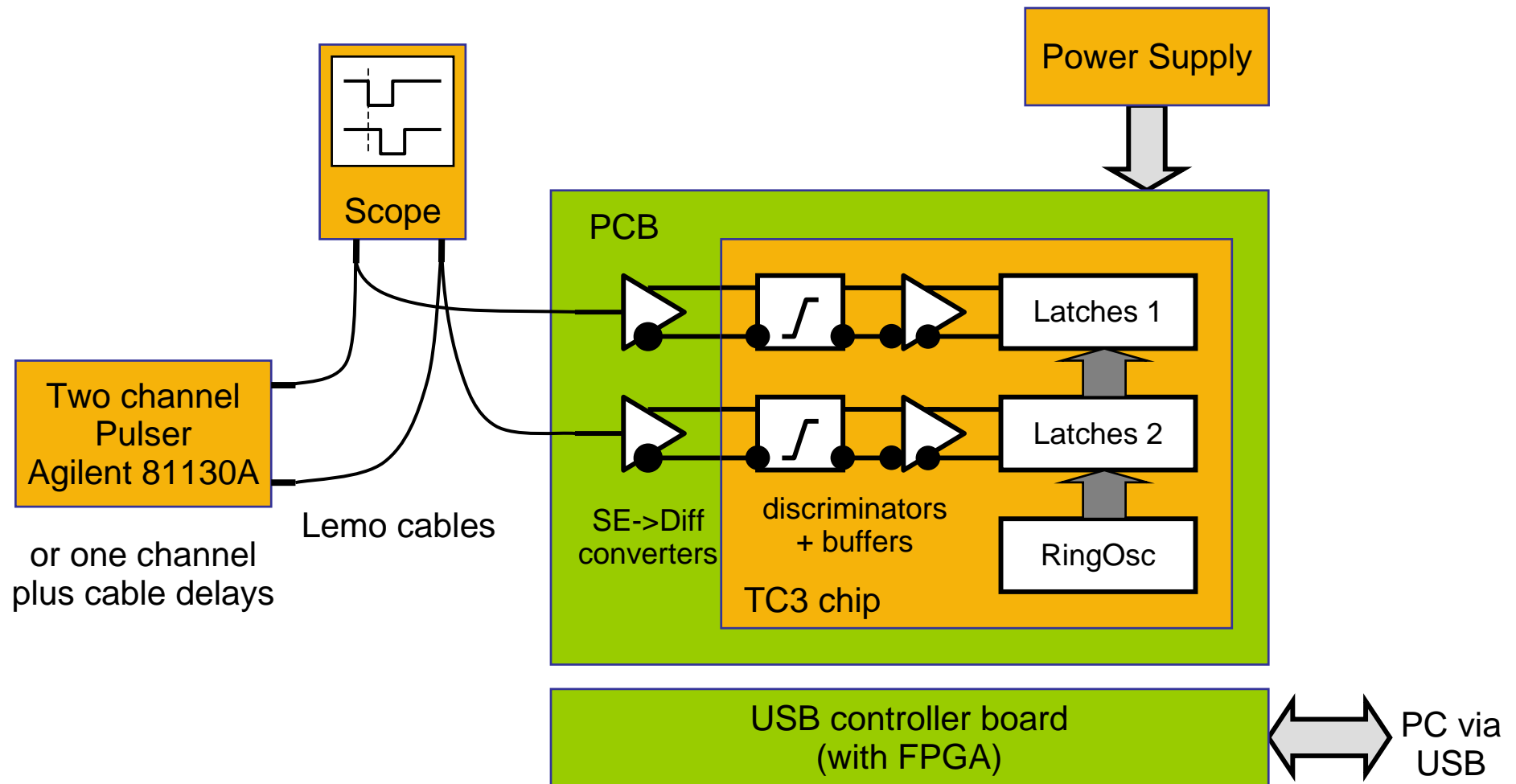- We have developed a very compact USB based test setup.





Measurements: Ring Oscillator Speed

  - 16 stage Ring oscillator speed can be measured on a scaled down digital output
- Speed can be tuned in a wide range as a function of bias current (per stage)
- Standard operation point: **150 ps / bin**




Hit bins for two different delays

  - Inject in the **two channels** with a constant (cable) delay
- VCO speed: **150ps / bin** $\Rightarrow \sigma_{\text{ideal}} = 43.3$ ps
- Plot time **difference** (here in bins) for two delays (**red**)
- Also plot fine grain result using (uncalibrated) 'slow' buffers (**green**)
- Note that measured **coincidence sigma** = $\sqrt{2}$ x **single channel sigma**




Bin occupancies (i.e. relative bin width)

 - Generate hits at random moments. Display counts for both channels
 - Equal time bin widths would give homogeneous bin occupancy
 - Shorter bins have lower occupancy




 - This measurement can be used to **correct for bin size**
- Note: variations are from transistor mismatch and stable in time – a chip ‘fingerprint’




Bin width correction

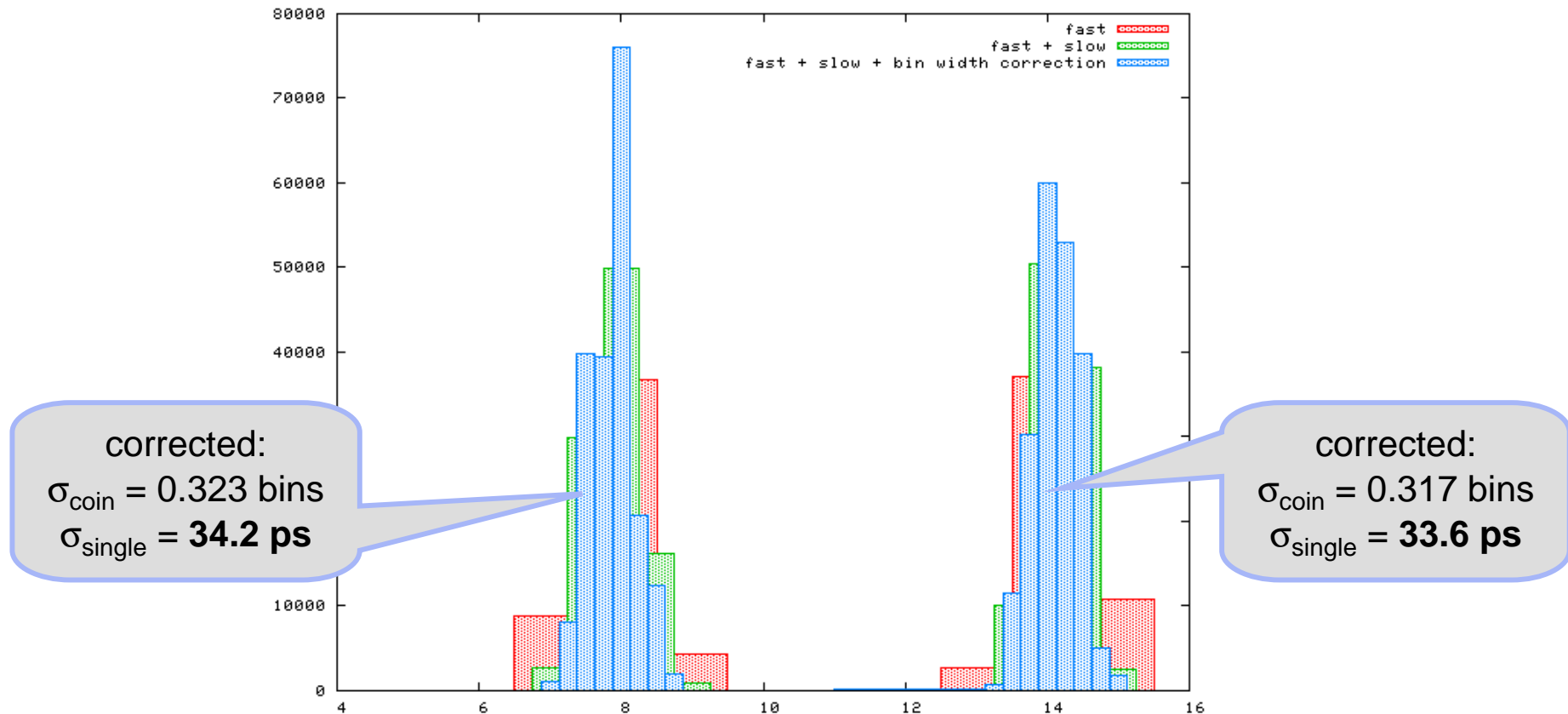- Use bin width information (fast / slow / mixed) for correction
- Maybe this result can still be optimized by adjusting the delay of the slow buffer...




 - Note that any non-linearities are included in this measurement!




Next Test Chip: UMC 0.18 μm (GSI Submission)

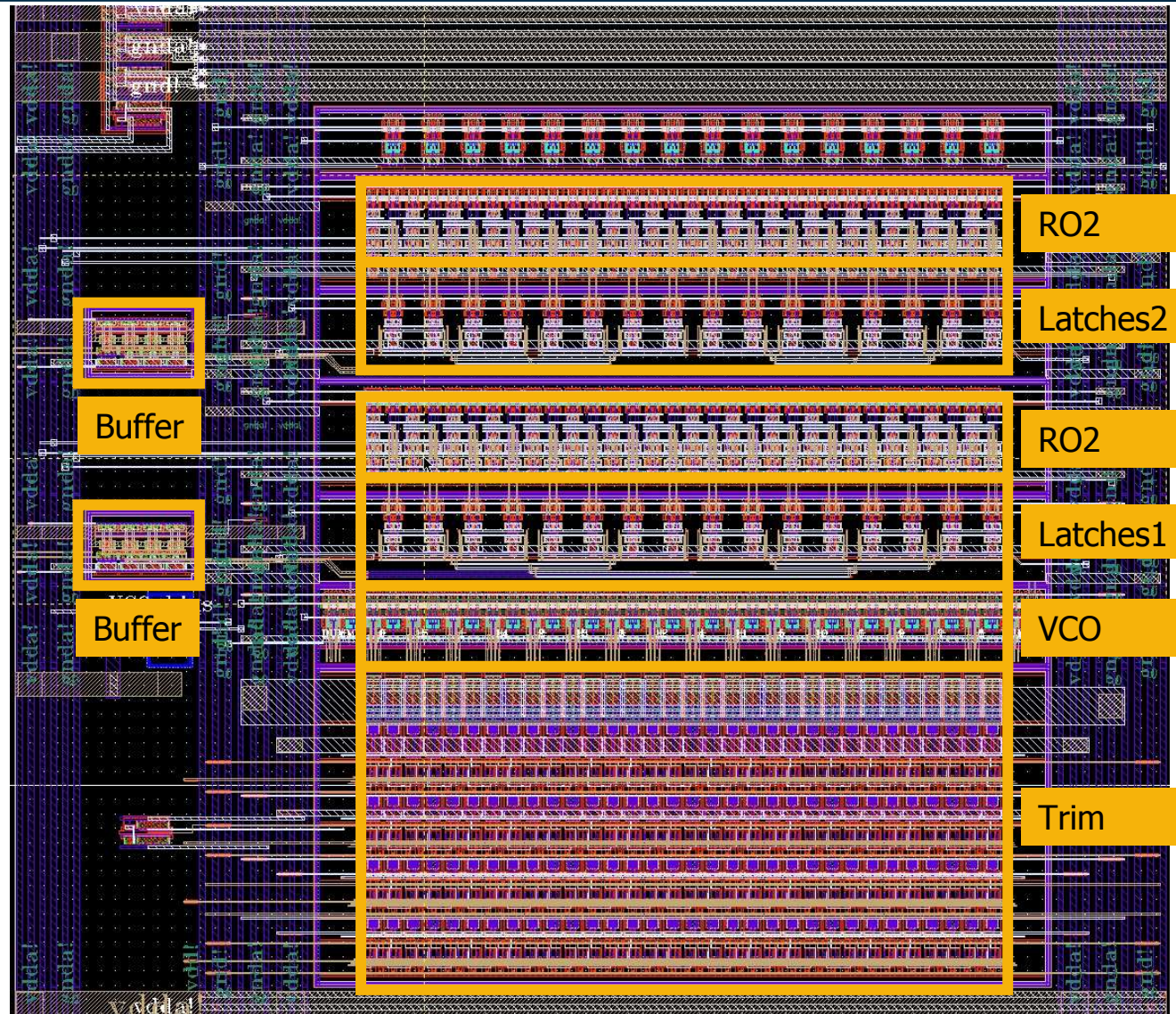- 16 stages
- 2 groups of latches
- VCO with or without delay trim
- VCO: 260 x 30 μm^2
- Trim: 260 x 120 μm^2



Layout:
VCO with Trim

 

Summary and outlook

- We pursue a **ring oscillator** approach using **differential logic**
- Single channel resolution $\sigma \sim \mathbf{35ps}$ already reached in 0.35 μm technology
- This fits well to the goal of 50ps (note: RPCs have 80ps time resolution)
- Advantages of the ring oscillator are:
 - stability (if locked to reference frequency with a PLL)
 - ‘infinite’ dynamic range (with wide ‘coarse’ counter)
 - very small dead time
 - fair power consumption (<15mA @ 2V per channel + VCO...)
- Expect factor ~ 2 improvement in 0.18 μm , i.e. $\sigma \sim \mathbf{25ps}$ (test chip has only fast bins).
- Next steps:
 - Test UMC chip (we will get it in 1 week!)
 - Increase speed, linearity, resolution – work is in progress

