 



# A Multi Channel ASIC for High Resolution Time Measurements




Schaltungstechnik  
und Simulation

Peter Fischer  
Michael Ritzert  
Martin Koniczek


# Overview of Circuit Concepts

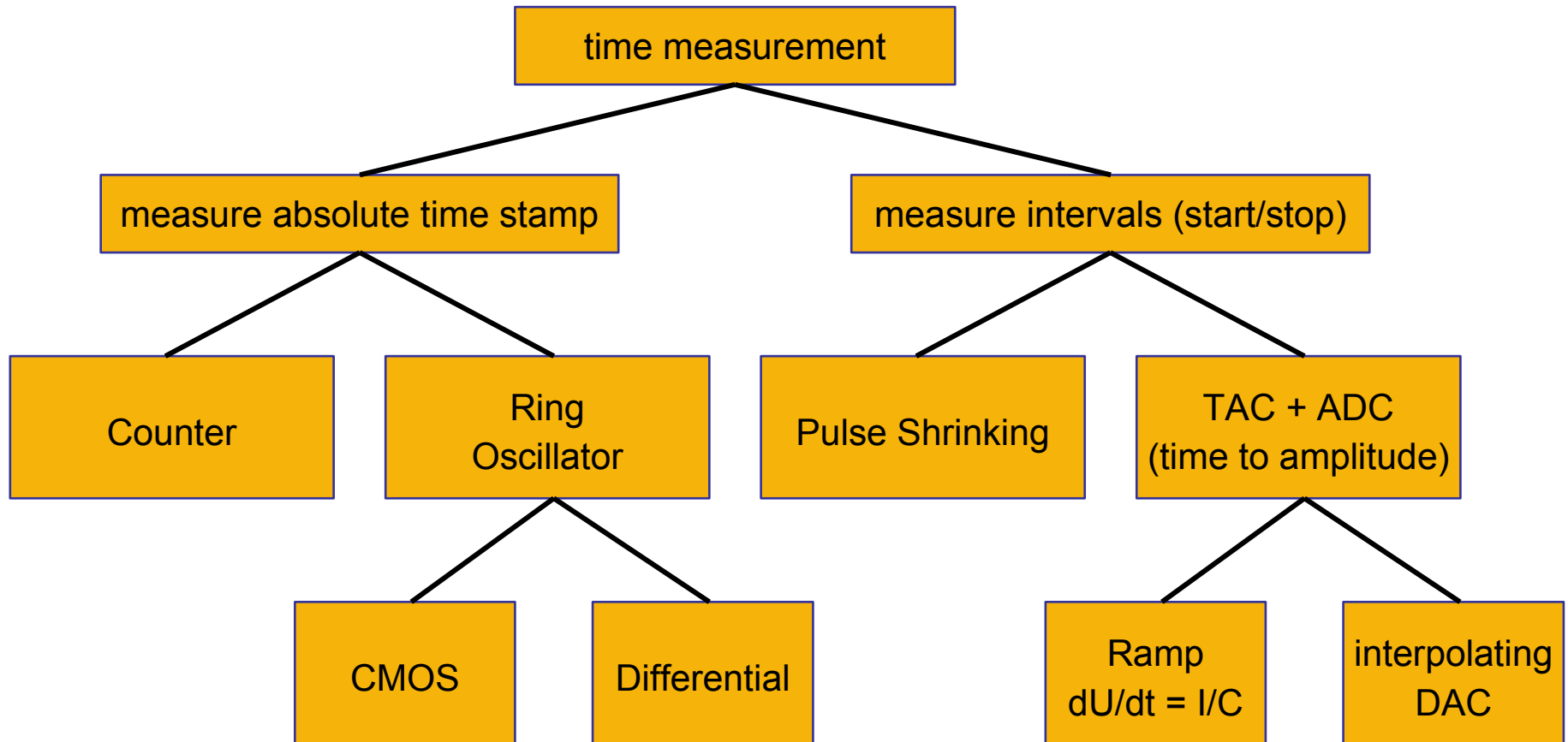

... and mixtures of these concepts

 

# Ring Oscillator: Principle

 

- Principle:

- a ring oscillator generates thermometer code time stamps. Needs overall inversion!
- a ("slow") coarse counter generates the MSBs
- input signal is used to latch values
- Ring oscillator can be locked to a reference clock with a PLL

+ fairly simple, "digital" design


+ infinite dynamic range

+ no calibration required (with PLL), guaranteed stability

- limited bin size (but several times better than with counter)

 
# Ring Oscillator: Design variations

- Resolution can be increased by:
  - using multiple channels with delayed stop signals
  - running several phase coupled ring oscillators
  - using slow / fast buffers between ring oscillator and latches
- Use "single ended" CMOS logic
  - simple
  - issues: supply sensitivity, ring oscillator frequency range, linearity (inversion!)
- Use differential logic
  - uncommon
  - more complex, if everything is done differentially
  - trimming simpler




 
# Design Issues

- Design goals are
  - minimal bin width = max. resolution (aim at  $\sigma = 20\text{ps}$ )
  - linearity
  - dynamic range
  - low dead time = high double hit rate (aim at 10 MHz)
  - low power (not so critical in Diamond: few channels, cooling possible, preamps and discriminators will be "high" power components)
  - easy calibration
  - stable operation (with temperature, power supply etc.)
  - multi-chip operation (maybe not required for diamond)
- Watch
  - matching between devices:  
better for larger devices, but that costs power and/or speed
  - radiation hardness
  - technology scaling (this favors "digital" designs)



 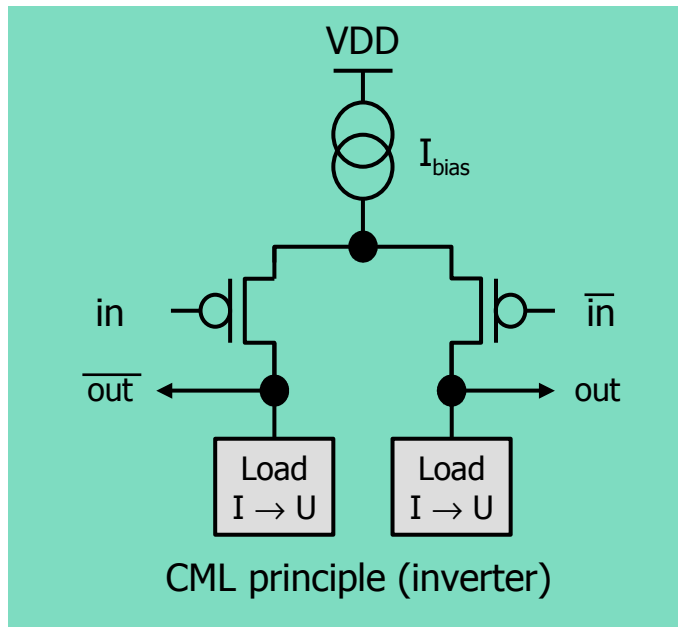
# Differential Logic

- Current  $I_{\text{bias}}$  is steered to left or right load circuit with a differential pair
- The load circuit converts to current step to a voltage step
- **'ideal' load** circuit:
  - The  $V_{\text{hi}}$ -level is fixed by the maximum possible input voltage to the switch block
  - The  $V_{\text{lo}}$ -level is fixed by the voltage swing required to 'fully' switch current in the switch block.
  - The plateau at  $\frac{1}{2}I_{\text{bias}}$  guarantees equal rise and fall times ( $C_{\text{load}}$  is charged/discharged with  $\frac{1}{2}I_{\text{bias}}$  )
- If  $V_{\text{hi}}$  and  $V_{\text{lo}}$  are independent of  $I_{\text{bias}}$ , the speed of the gate can be varied significantly with  $I_{\text{bias}}$



 
# Submission History

- **TC3:** AMS 350nm.  
Results presented here last year.  
Timing resolution  $\sigma \approx 35\text{ps}$ .
- **TC\_UM1:** First UMC 180nm submission.  
Run paid for by GSI.  
Timing resolution  $\sigma \approx 25\text{ps}$ .
- **TC\_UM2:** Current chip. UMC 180nm.



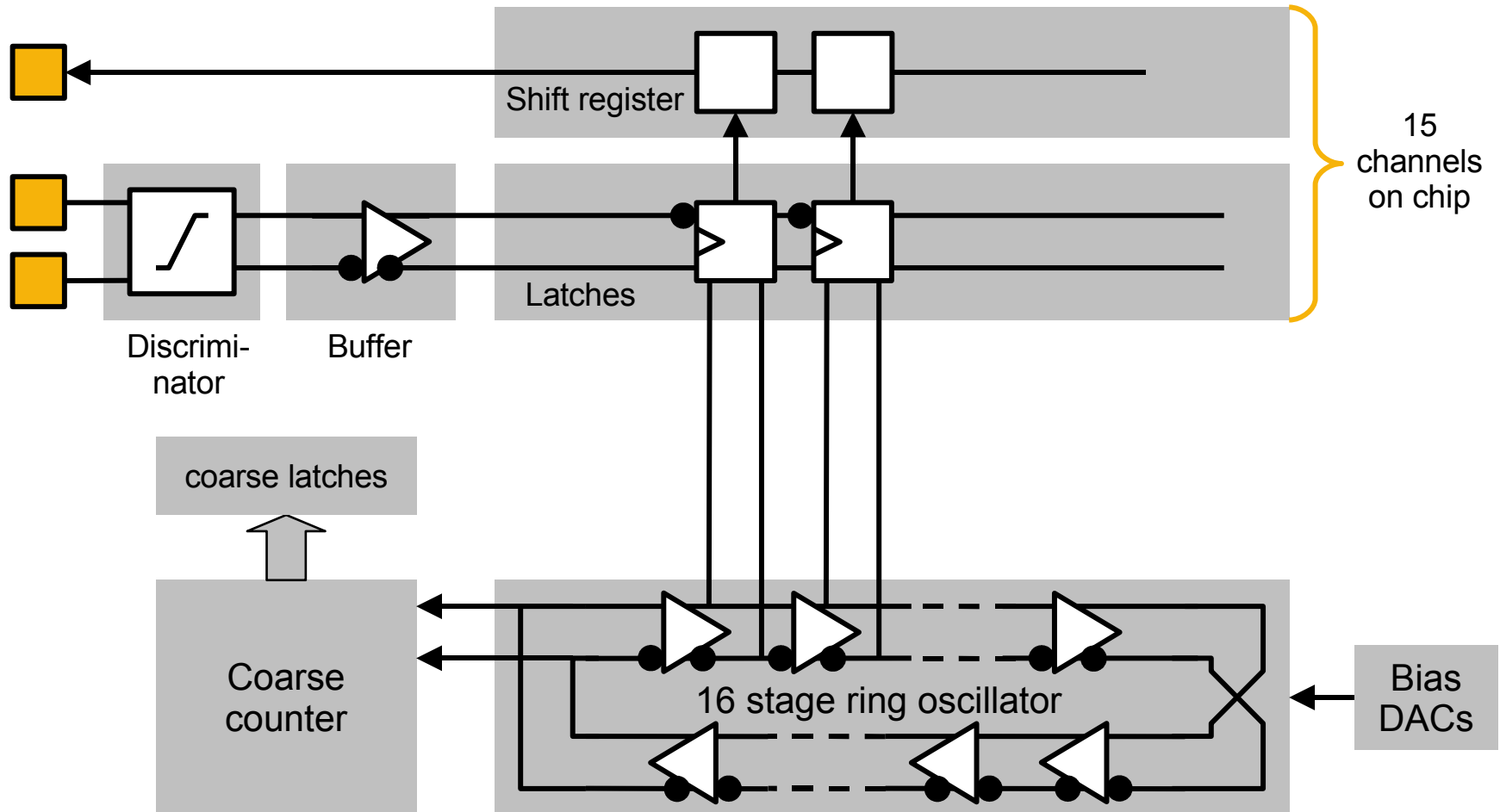
# TC\_UM2 Block Diagram

- Block diagram shows only relevant parts
- Note that the differential inputs have an additional (analog) discriminator on this chip







# TC\_UM2 Layout

 

- Size: 3.24x3.24mm<sup>2</sup>
- 15 Channels

 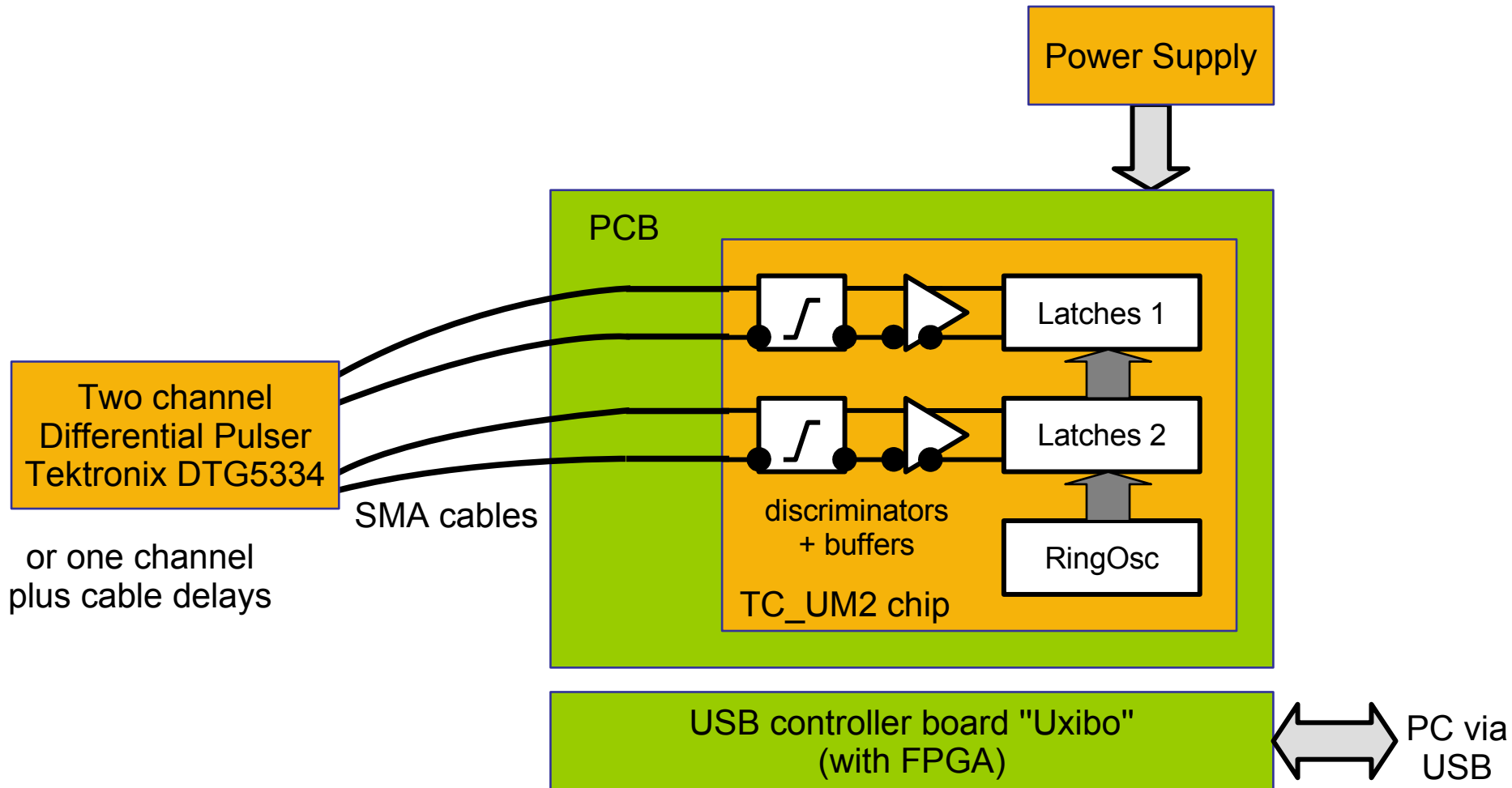
# Test Setup

- We have developed a very compact USB based test setup.




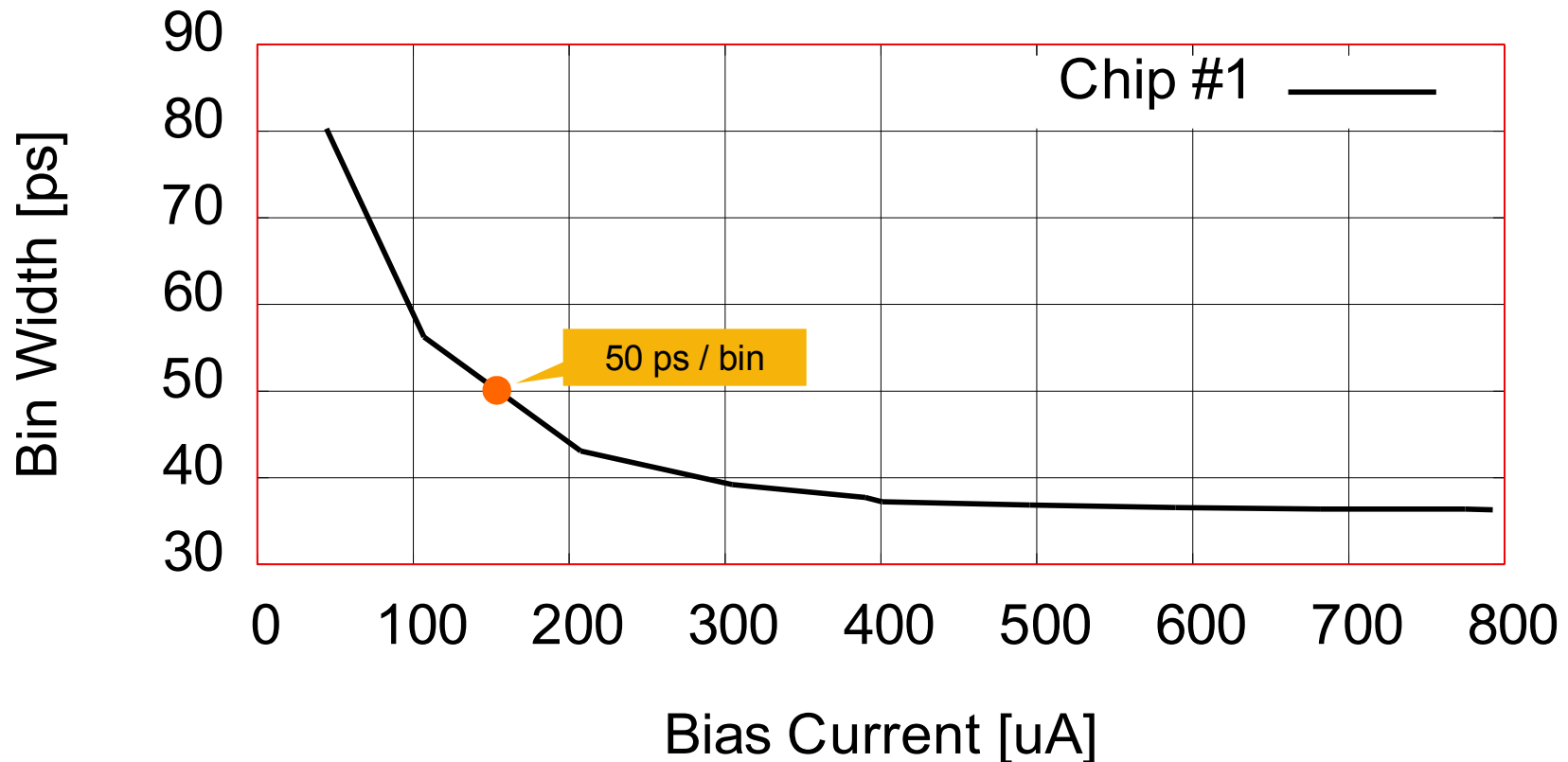
# Measurements: Ring Oscillator Speed

- Accurate measurement of the VCO speed possible on a full-speed debug output
- Tuning range ~37 - 80 ps
- Standard operating point: **50 ps binwidth @ 160uA per stage** (from a 1.8V supply)


 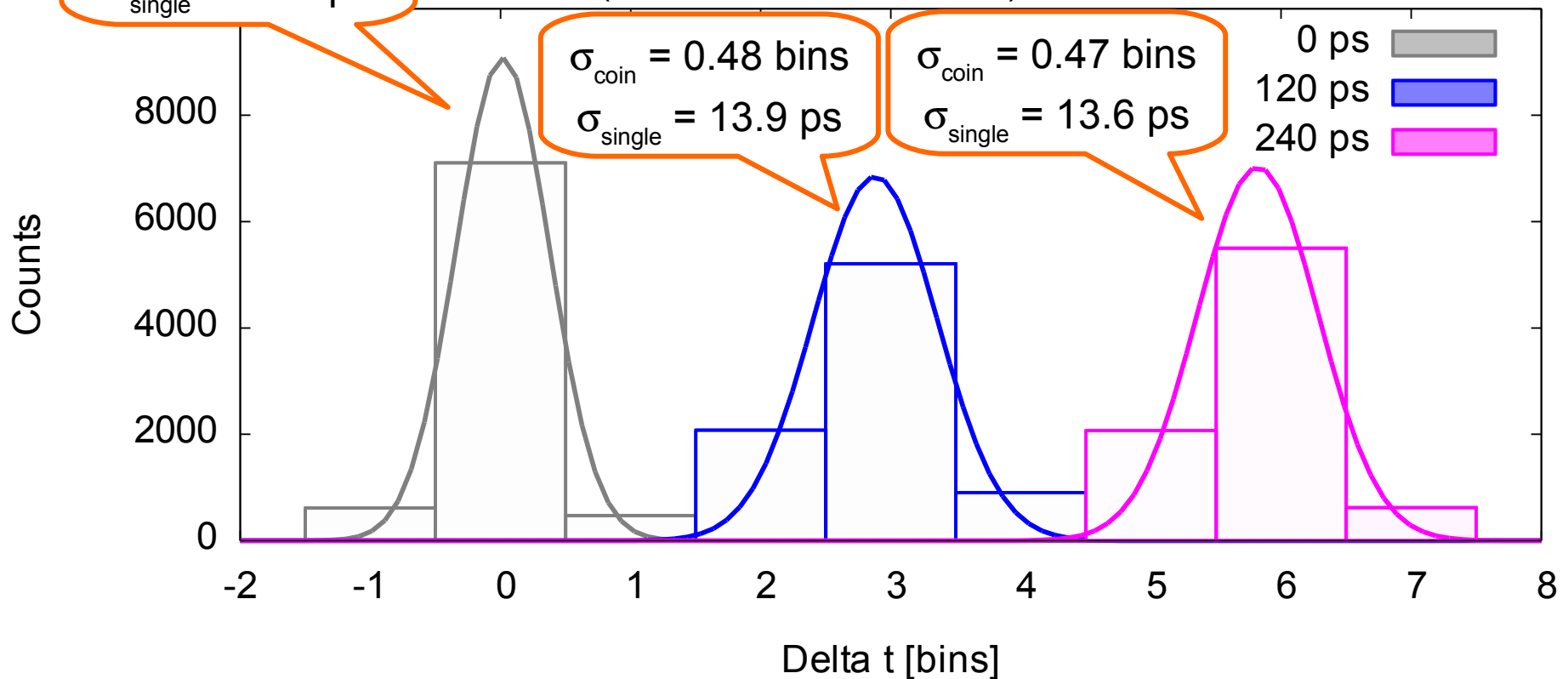
# Hit bins for different delays

- Plot time **difference** (here in bins) for different delays
- Note that measured **coincidence sigma** =  $\sqrt{2}$  x **single channel sigma**
- VCO speed was **~41ps / bin** for this measurement
- Plot shows results that have been **corrected for different bin sizes** (from transistor mismatch)



# Summary

- We pursue a **ring oscillator** approach using **differential logic**
- Single channel resolution  $\sigma < 20\text{ps}$  **available today** in 180nm technology  
All non-linearities are included in this figure!
- Advantages of the ring oscillator are:
  - stability (if locked to reference frequency with a PLL)
  - "infinite" dynamic range (with wide "coarse" counter)
  - very small dead time
  - fair power consumption (<20mA @ 1.8V per channel + VCO)

