



Diamond detectors in FOPI

M.Ciobanu, M.Kis, A.Schüttauf



Outline

- FOPI's constrains on a start counter
- Timing relevant factors
- Diamond detectors
 - Heavy ion case Z>6
 - Proton case
- Summary and Outlook



FOPI's start counter

Heavy ion case:

For C-Au ions we need a start-counter better then σ_{ts} < 50 ps, with tails smaller 1 ‰ @ 1MHz. To ensure the Pion-Kaon id up to 1 GeV/c.

Proton case:

The proton experiments hunt for rare event and will be operated at SIS space charge limit, with an estimated rate of 10 MHz. For this an experiment a start resolution below σ_{ts} < 70 ps is needed.



Theory



What determines the timing ?





Simplest case a D+BBA

$$i^{2}_{nRi} / \Delta f = 4k \cdot T / Ri$$
$$i_{Tr}(t) = I_{0} e^{-t/\tau}$$
$$i_{Tr}(t) = Qii(e,h) / \tau \cdot e^{-t/\tau}$$

$$S = V_{Sin} = i_{Tr}(0) \cdot R_i = Qii(e,h)/t \cdot R_i = Qii(e,h)/C_D$$

$$N^2 = V^2_{Nin} = i^2_{nRi} / \Delta f \cdot R^2_i \cdot f_u \pi / 2 = 4k \cdot T \cdot R_i \cdot BW_N = k \cdot T / C_D$$

$$BW = f_u$$

$$BW_N = \pi / 2 \cdot f_u$$

$$\sigma_t = \sigma_n / (dv/dt)$$

$$t_{rA} = 0.35 / BW_A, dv/dt = 0.8 \cdot V_{Sin} / t_{rA} = 2.28 \cdot Q_{ii}(e,h) / C_D \cdot BW_A$$

Energy measurement: S/N

 $S/N = Qi(e,h)/\sqrt{k \cdot T \cdot C_D}$

Timing measurement: N/(dv/dt)





A more realistic case in RF

Add a realistic noise factor F for RF applications:

F= Total noise/source resistor noise (Rs)

$$F = \frac{e_{nRS}^{2} + e_{neq}^{2}}{e_{nRs}^{2}} = 1 + \frac{i_{nA}^{2} \cdot R_{S}^{2} + e_{nA}^{2}}{e_{nRs}^{2}}$$
$$i_{nA}^{2} \cdot R_{s} + e_{nA}^{2} = (F - 1) \cdot e_{nRs}^{2}$$
$$i_{neq}^{2} = (F - 1) \cdot i_{nRs}^{2}$$
$$i_{neq}^{2} - (F - 1) \cdot i_{nRs}^{2}$$
$$i_{neq}^{2} - (F - 1) \cdot i_{nRs}^{2}$$

For good energy measurement
we have to:
1) Minimize:
$$C_D$$
, T, F
2) Maximize: $Q_{ii} \rightarrow CSA$

For good timing measurement we have to: 1) Minimize: C_D, T, F 2) Maximize: BW_A → BBA



Simulations



Three cases for simulations





Simulations for signal shapes





AC-simulations





Simulations on the timing



Setups Electronics Measurements



Setups for the MOS-follower





Two systems are prepared for a MIP (proton) measurement:

- 1) SC-DD, D=2mm, h=0.15mm, four quadrants, 4 capacitive buffers on each ensemble,
- 2) Two FEE1 are modified as a second stage for the analog data processing.

Waiting for beam and change the MOSFET to a lower C_{G1-S}<1pF !



SCD with PADI for rate tests

PADI = Preamplifer Discriminator An ASIC based amplifier for timing measurements.





PADI- pulser measurements





First PADI PCB for SCD

Connection's with SC Diamond Pixel Detector







Rate dependence of PADI





The Heavy Ion case !





A Diamond-PADI-Start

Start

PADI



HALO

Level adapter



Diamond including the Start and HALO detector for beam monitoring. The readout is done by PADI.

This setup needs more R&D to optimize the bonding, impedance and signal transport.

Too ambitious but the right way!!



Results with PADI



Pros:

Using PADI to read out a PCD, we reached σ_{td} <45 ps in relation to a plastic scintillator.

Cons:

The connection (bonding) is critical and introduced impedance problems which have to be solved In the next step.

Up to now, low rate only (1 kHz)!



Results with FEE1 (test'08)



Pros:

Using FEE1 to read out a PCD, we reached σ_{td} <41 ps in relation to a plastic scintillator.

Cons:

The FEE1 is not suitable for MIPs. At higher rates we see the tail from the plastic (>5kHz).



Results with FEE1 (run '08)





How to build a MIP start ?

Diamond:

A SC diamond with a $5x5mm^2$ metallization at a thickness of d=0.4 mm has capacitance of C_D=3 pF.

We can decrease the detector capacitance by dividing the diamond into NxN pixels:

 N
 2
 3
 4

 C_D pixel
 0.75pF
 0.33pF
 0.187pF

For other d, for example d1=d/2, the capacitances are two times higher.

Electronics:

- TAmp which HADES used (BFG410W) with a 22 GHz BW: N_{F} ~1dB, C_{e} ~0.4pF, C_{re} ~50fF.
- MOS-Follower to be used in the FOPI Proton tests (BF998) has: C_{G1-S}~2.1pF, C_{rt}~25fF (reverse transfer capacitance) and the frequency domain 1GHz.
- NINO-Low Capacity (LC) in 130 µm technology.
- PADI-LC in 180 µm technology.



NINO-LC for a pixel start

130 nino circuits

 2 versions of NINO architecture implemented in a 0.13 μm technology

P. Jarron CERN PH

LCO version (for Cin ~ 200 fF)

- Noise < 1000 e- rms
- Rising time < 500 ps rms
- Power consumption : 300 μW
- Tunable threshold (0 to 4 fC)
- Differential output





HCO version (for Cin ~ 10 pF)

- Noise < 4000 e- rms
- Rising time < 200 ps rms
- Power consumption : 3 mW
- Tunable threshold (0 to 20 fC)
- Differential output



P.Jarron CERN PH

Using a timing ASIC for a silicon readout !

NINO Electronic Jitter < 40 ps





Scatter plot of time jitter versus pulse width

Jitter vs. input charge

100fF calibration capacitance,



PADI-Low Capacitance (LC)





A possible MIP diamond start



4x4 pixel SCD 4 PADI (LC) 4 DANTE



4x4 pixel SCD 2 NINO (LC) 4 DANTE





Summary & Outlook

Summary

- In our current understanding we need a low capacitance (<0.2 pF) diamond followed by a low capacitance amplifier (<0.4 pF).
- In simulations we understand our timing behavior within the current setups.
- We tested different electronic readout concepts during 3 years:

	PCD	SCD
A) FEE1 (DBA)	40	450
B) CSA		250
C) MOS-follower	(40)	(80)
D) PADI	45	?

- In real experimental conditions the diamonds are not fully understood but timing ~ 50 ps !
- SC diamonds died during runs frequently !!
- The main conclusion from the experimental runs:

Don't make it to complicated !!!

Outlook

- From the latest simulations and the most recent ASIC developments at CERN (NINO-LC) and GSI (PADI-LC) the development of an Diamond-ASIC is possible and should be done.
- For FOPI an 4x4 pixel SC-Diamond (5x5 mm²) with an C_D of 0.18 pF is reasonable.
- PADI is in principle capable to be redesigned, at the amplifier stage, to have 16 times higher sensitivity at a 3-5 times higher noise level.
- Using DANTE as a digitizer we could be compatible for CBM as well.

We would like to thank the whole detector—lab crew for the support and help in preparing the diamonds and in participating their beam-times.





Old stuff



 Timing measurements with CVD diamonds, Tomica Porobić, RBI Zagreb, Croatia, for FOPI collaboration, talk at NORHDIA Meeting, Sept.2006

FEE1



FOPI-FEE1 1. 4 Channels AC Amp., LE Disc., 4*OR, THR and GAIN man. adj.

2. +6V, +12V, -6V 1.85 W/Ch. 3. Dim.: 110mm * 95mm 4.INP.: 4 LEMO 1 LEMO TEST 5.OUT.:4 NIM for TIME 4 LEMO Amplitude 1 LEMO OR 6.AC: - GAIN ~ 0-200 - Bandwidth ~ 1GHz - Noise ~ 20µV - Rise Time ~ 350ps 7. Disc.:- Noise ~ 40µV - Rise Time ~ 500ps - Res. Jitter ~4.8ps 8. Time Res.: 30-10-5-4-4 [ps]

PADI



CBM-PADI

- Time res.(@10mV) [ps] < 10</p>
- Gain ~ 60
- Bandwidth [MHz] ~ 180
- Linear range [mV] ~ -5 to 5
 - CTRR [dB] ~ 26 40
- CMRR [dB] > 40
- Input impedance [Ω] ~ 48 58
- Power [mW/Ch] ~ 31

PADI-parameter

- DC Power Consumption:		31[mW/ch]	
- DC Threshold Calibration:			
The transfer characteristics from	the threshold voltage		
applied to PADI terminals to ene	ergy output is:	0.334 (σ=0.022)	
- Input impedance measureme	nts:	Ζ_{ΙΝΡ}[Ω]	
1. AC method : Questionable!		27-96	
2. TDR method adapted for low le	vel signals, with "T"	35-67	
3. TDR adapted for low level signa	als, with a directional coupler	42-59	
4. Short pulse method for low leve	el signals, directional coupler	48-58	
- Crosstalk measurements:	CTRR32	CTRR31	
PADI (AC @75MHz) [dB]	25-30	22-27	
PADI Pulse Meas. [dB]	>40		
- Common Mode Rejection Rati	o Measurement		
PADI Pulse Meas. [dB]	26-40		



DANTE (Double DLL)



- **CBM-TDC** Double DLL core DANTE@156.25 MHz Bin width 50 ps → 14.4 ps Process: UMC 0.18 µm 4-16 channels LVDS input Multi-hit with no DT DP: 3.2 ns ToT: min. width 50 ps DT: 0
- CT: ?
- INL: < 0.5 LSB (25 ps)</p>
- Power con.: 30 mW/ch

Rate dependence II







To use the new NINO developed at CERN is a good idea, but we must be carefully with the input impedance; if the new NINO has 500hms like the old NINO, I am not very sure of success.

The MOS used in FOPI Proton tests and in MOS-follower simulations (BF998) has: CG1-S~2.1pF, Crt~25fF (reverse transfer capacitance) and the frequency domain 1GHz.
The transistor used in simulations (BFG410W) is a 24GHz transistor having: NF~1dB, Ce~0.4pF, Cre~50fF

- In the FOPI Proton tests we used a SC DVD diamond (5x5mm²) and a metallization of 2.6x2.6mm².

With this configuration we have a $C_D \sim 1 \text{pf}$ and the parasitic capacitance at the input of CSA of $C_P \sim 5.5 \text{pf}$.

In comparison the HADES case he detector capacitance is 4 times smaller $C_{\rm D}{\sim}$ 0.25 pf .



Schematic view of the board



PADI Test Plate

LVDS - PECL Adapter



Schematic view of the setup



The scaler was programmed to measure rates in 1ms time slices. The setup was optimized for high rate measurements: For each channel the maximal rate is 1.5×10^8 [hits/s]

A beam sweep with C¹² ions



The carbon ions have an initial energy of 88.83MeV/u with constant focus (#7) and intensity (#1).

The sweep covered an area of 120mm x 20mm with 671 points